

## Efficiency in class-B amplifiers


(or... how hot does it really get).

For class-A amplifiers, we just looked at the quiescent condition — no signal.

It is different with a signal, but not much.


Class-B amplifiers have very low quiescent dissipation, but it goes up a lot with a signal.

Consider the same 50 watt amplifier...

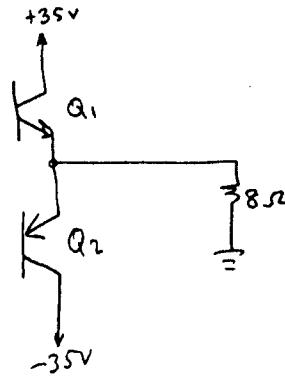

Suppose it is actually delivering 50 watts to the load.
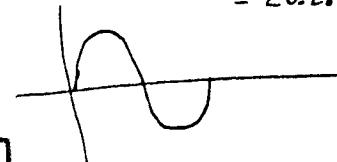
$$\text{Load voltage} = 20 \text{ RMS} \\ = 28.28 \text{ peak}$$



Homework —

Chapter 8


$$\text{Load current} = 2.5 \text{ amp.} \\ = 3.536 \text{ peak.}$$

1


But Voltage across device is  $V_{\text{power}} - V_{\text{load}}$ .

Take some points --

V <sub>out</sub>	V <sub>ai</sub>
0	35
28.3	6.7
-28.3	63.3

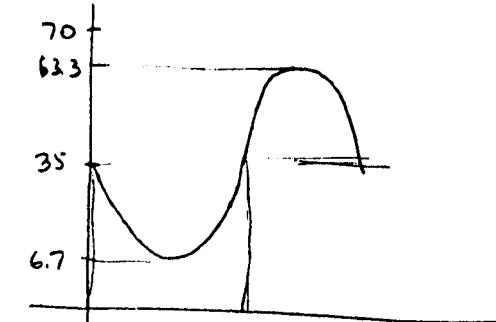

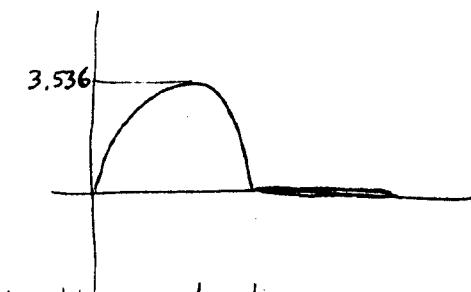Current is the load current, halfwave rectified



Instantaneous power is the product

P <sub>in</sub>	V <sub>out</sub>	V <sub>ai</sub>	I <sub>ei</sub>	P <sub>load</sub>	P <sub>ai</sub>
0	0	35	0	0	0
21.88	15	30	.625	3.125	18.75
43.75	10	25	1.25	12.5	31.25
65.63	15	20	1.875	21.13	37.5
87.50	20	15	2.5	50	37.5
109.4	25	10	3.125	78.13	31.25
131.3	30	5	3.75	112.5	18.75
153.1	35	0	4.375	153.1	0
28.3	6.7	3.536	100	23.7	
17.7	17.7	38.28	38.28	38.28	

Q1 power  
Waveform

Take average value  $\rightarrow \approx 15$  watts.

and  $\approx 15$  watts in other device.

Total  $\approx 30$  watts.

Calculations:

$$V_{out} = 28.3 \sin(\omega t)$$

$$V_{Q1} = 35 - V_{out}$$

$$= 35 - 28.3 \sin(\omega t)$$

$$I_{out} = 3.54 \sin(\omega t)$$

$$I_{Q1} = \begin{cases} 3.54 \sin(\omega t) & V > 0 \\ 0 & V < 0 \end{cases}$$

$$P_{out} = V_{out} I_{out}$$

$$= (28.3 \sin(\omega t)) * (3.54 \sin(\omega t))$$

$$= 100 \sin^2(\omega t)$$

$$P_{Q1} = V_{Q1} I_{Q1}$$

$$= (35 - 28.3 \sin(\omega t)) * \begin{cases} 3.54 \sin(\omega t) & V > 0 \\ 0 & V < 0 \end{cases}$$

$$P_{Q1} = \begin{cases} 124 \sin(\omega t) - 100 \sin^2(\omega t) & V > 0 \\ 0 & V < 0 \end{cases}$$

Input power      Power delivered to load

(3)

Avg power dissipated =

$$\frac{1}{2\pi} \left( \int_0^\pi (124 \sin(\omega t) - 100 \sin^2(\omega t)) d(\omega t) + \int_{-\pi}^0 0 d(\omega t) \right)$$

$$= \frac{1}{2\pi} \left( 124 (\cos(\pi) + \cos(0)) - 100 \left( \left( \frac{\pi}{2} - \frac{1}{4} \sin(2\pi) \right) - \left( \frac{\pi}{2} - \frac{1}{4} \sin(-2\pi) \right) \right) \right)$$

$$= \frac{1}{2\pi} (124(2) - 100(\frac{\pi}{2}))$$

= 14.47 watts  $\rightarrow$  each device

or 28.9 watts total

(4)

$$\int \sin^2 dx = \frac{x}{2} - \frac{1}{4} \sin 2x \quad (\text{cc})$$

Power in

$$= \underbrace{\frac{1}{2\pi} \int_0^\pi 124 \sin(\omega t) d\omega t}_{NPN} + \underbrace{\frac{1}{2\pi} \int_{-\pi}^0 124 \sin(\omega t) d\omega t}_{PNP}$$

$$= \frac{1}{2\pi} (124(1+1)) + \frac{1}{2\pi} (-124(-1-1))$$

$$= 39.5 + 39.5 = 79 \text{ watts.}$$

$$\text{Efficiency} = \frac{50}{79} \approx .63 \rightarrow 63\%$$

(at 50 watts)

## Thermal considerations

Usually, you will find a spec for thermal resistance.

$$\Theta = \frac{\text{°C}}{\text{watts}} \leftarrow \text{temperature difference.}$$


It's covered in detail in Thermodynamics.

For here, think of it like a circuit -

Heat sources are like currents.

Temperatures are like voltages.

You will also find a "derating curve".

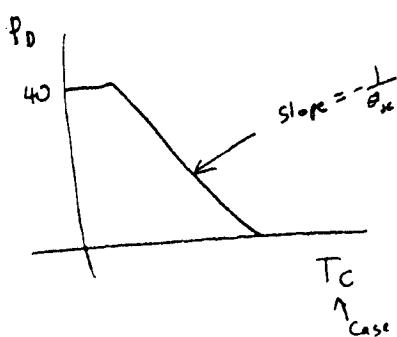

Example -

A 2N2219  
is dissipating .5 watt.  
With ambient temp = 30°C.

What is the case temp?  
What is junction temp?

From data sheet ..  
 $\Theta_{JA} = 219 \frac{\text{°C}}{\text{W}}$

$$\Theta_{JC} = 58 \frac{\text{°C}}{\text{W}}$$

$$\rightarrow \text{Implies } \Theta_{CA} = 161 \frac{\text{°C}}{\text{W}}$$

5 °C

Example - continued

$$\Theta_{JA} = 219 \frac{\text{°C}}{\text{W}} \rightarrow 219 \frac{\text{°C}}{\text{W}} * .5 \text{W} = 109.5 \text{ °C} \approx 110 \text{ °C}$$

↑  
junction temp rise.

$$\text{junction temp} = T_A + T_{rise} = 30 + 110 = \underline{\underline{140 \text{ °C}}}$$

$$\Theta_{CA} = 161 \frac{\text{°C}}{\text{W}} \rightarrow 161 \frac{\text{°C}}{\text{W}} * .5 \text{W} = 80.5 \approx 81$$

$$\text{case temp} = T_A + T_{CA} = 30 + 81 = \underline{\underline{111 \text{ °C}}}$$

If max junction temp is 200°C, ambient temp = 40°C  
What thermal resistance is required for our 50 watt amp?

Power dissipation  $\approx$  15 watts per device

$$T_{Diff} = 200 - 40 = 160$$

$$\Theta_{\text{required}} = \frac{160 \text{ °C}}{15 \text{ watts}} = 10.67 \frac{\text{°C}}{\text{Watt}}$$

JA  
↑  
junction to  
ambient

$$\text{MJ802 has } \Theta_{JC} = .875 \frac{\text{°C}}{\text{W}}$$

need heat sink  $10.67 - .875 = 9.8 \frac{\text{°C}}{\text{Watt}}$   
- - - - -  
Tip 31 is cheaper and rated 40 watts. Will it work?  
Max jct temp = 150°C,  $\Theta_{JC} = 3.125 \frac{\text{°C}}{\text{W}}$

$$\Theta_{req} = \frac{150 - 40}{15} = \frac{110}{15} = 7.33 \frac{\text{°C}}{\text{Watt}} - \text{Yes - need heatsink -}$$

$$7.33 - 3.125 = 4.2 \frac{\text{°C}}{\text{W}}$$

More than twice the heat sink as MJ802

6 °C