



①
 μ
 $K_P = 20 \mu$
 $\lambda = 0.01$
 $V_{T0} = 1$

Stage 2 - Gain = -100

M1 - Mirror - Calculate r_o ... $V_{DS} = 20$ $I_D = 100 \mu A = 10^{-4}$

$$r_o = \frac{1}{\lambda I_D} = \frac{1}{(0.01)(100 \mu)} = \frac{1}{10^{-2} \cdot 10^{-4}} = \frac{1}{10^{-6}} = 10^6$$

M3 - Calculate r_o ... $V_{DS} = 10$ $I_D = 100 \mu A$ $r_o = 10^6$

$$r_{Load} = 500 \Omega$$

$$gain = -g_m R_L \rightarrow g_m = \frac{-gain}{R_L}$$

$$g_m = \frac{+100}{500 \text{K}} = 2 \times 10^{-4}$$

Stage 3:

$$R_o = 200 \Omega = \frac{1}{g_m} \Rightarrow g_m = .005 = \sqrt{2 K_P \frac{W}{L} I_{DQ}}$$

$$= \sqrt{(2)(20 \times 10^{-4}) \frac{W}{L} (10 \times 10^{-3})}$$

$$5 \times 10^{-3} = \sqrt{(400 \times 10^{-7}) \frac{W}{L}}$$

$$2.5 \times 10^{-5} = 4 \times 10^{-7} \frac{W}{L}$$

$$62.5 = \frac{W}{L}$$

$$L = 1 \mu \quad W = 62.5 \mu$$

Calculate V_{GS} -

$$I_D = K V_{GS}^2$$

$$2K = K_P \frac{W}{L}$$

$$= (20 \times 10^{-4})(62.5)$$

$$= 1.25 \times 10^{-3}$$

$$K = 6.25 \times 10^{-4}$$

$$V_{GS}^2 = \frac{I_D}{K} = \frac{1 \times 10^{-2}}{6.25 \times 10^{-4}} = 16$$

$$V_{GS} = 4$$

$$V_{GS} = 5$$

~~$$= \sqrt{2 K_P \frac{W}{L} I_{DQ}}$$

$$= \sqrt{(2)(20 \times 10^{-4}) \frac{W}{L} (10^{-4})}$$

$$= \sqrt{40 \times 10^{-10} \frac{W}{L}}$$

$$= \sqrt{4 \times 10^{-9} \frac{W}{L}}$$

$$4 \times 10^{-9} = 4 \times 10^{-9} \frac{W}{L}$$

$$\frac{10^{-9}}{10^{-9}} = \frac{W}{L} = 10$$

$$= \sqrt{2 K_P \frac{W}{L} I_{DQ}}$$

$$= \sqrt{2(5 \times 10^{-4}) \frac{W}{L} (10^{-4})}$$

$$= \sqrt{10 \times 10^{-10} \frac{W}{L}}$$

$$= \sqrt{10^{-9} \frac{W}{L}}$$

$$4 \times 10^{-9} = 10^{-9} \frac{W}{L}$$

$$\frac{4 \times 10^{-9}}{10^{-9}} = \frac{W}{L} = 40$$~~

$$V_{GS} \dots$$

$$I_D = K V_{GS}^2$$

$$2K = K_P \frac{W}{L}$$

$$= (5 \times 10^{-4}) \frac{W}{L}$$

$$= 200 \times 10^{-8}$$

$$= 2 \times 10^{-4}$$

$$K = 1 \times 10^{-4}$$

$$V_{GS}^2 = \frac{I_D}{K} = \frac{10^{-4}}{10^{-4}}$$

$$= 1$$

$$V_{GS} = 2$$

Diff -am.

$$I = 10 \mu A$$

Current mirror - $I = 5 \mu A$ each. size = $\frac{10}{10}$

$$M6: V_{DS} = 2$$

best way -- size so $V_{GS} = 2$
 $(V_{GS} = 1)$

$$I_D = K V_{GS}^2$$

$$5 \mu = K$$

$$2K = 10 \mu = K_p \frac{W}{L}$$

$$10 \mu = 5 \mu \frac{W}{L}$$

$$\frac{10 \mu}{5 \mu} = \frac{W}{L}$$

then need to consider lambda.

M5, M6

$$r = \frac{1}{\lambda I_D} = \frac{1}{(.01)(5 \mu)} = \frac{1}{10^{-2} 5 \times 10^{-6}} = \frac{1}{5 \times 10^{-8}} = 2 \times 10^7 = 20 \text{ meg}$$

M8:

$$r = \frac{1}{\lambda I_D} = \frac{1}{(.01)(10 \mu)} = 10 \text{ meg}$$

3

```

print four v(10)
plot tran v(10)
modify load=1k
generator freq=100 amp1=.01
fourier 100
freq=10
amp1=.0005
generator freq=1k amp1=.01
fourier 1k
freq=10k
amp1=.01
fourier 10k
freq=100000
amp1=.00005
fourier 10k

**** even higher level
plot tran v(10) (-10,10)
generator freq=100 amp1=.1
fourier 100
generator freq=1k amp1=.1
fourier 1k
generator freq=10k amp1=.1
fourier 10k
generator freq=100000 amp1=.00005
fourier 10k

```

distortion

7