

EE 420 - Electronics - 2

Name _____

Number _____

1 _____

2 _____

3 _____

4 _____


Row total _____

Scaled _____

Put your name only
on the cover.

Put your number on
all pages.

① Here is a power stage ----

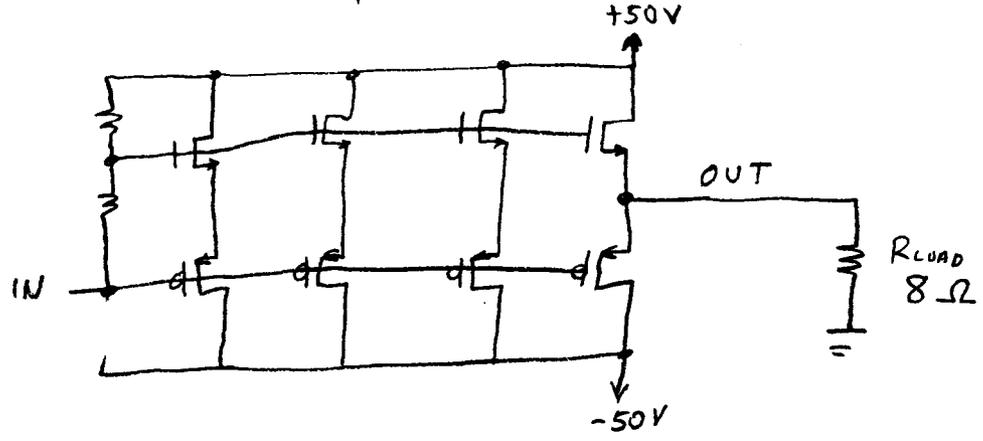

Assuming that there is 2 volts across the devices at clipping -

(a) What is the maximum sine wave power?

(b) What is the worst power dissipation with a square wave?


Total →

per device →

(c) What is the efficiency with the signal used in b?

(d) What device transconductance is necessary for 2 volts across the device at clipping?

2) Here is an incomplete op-amp

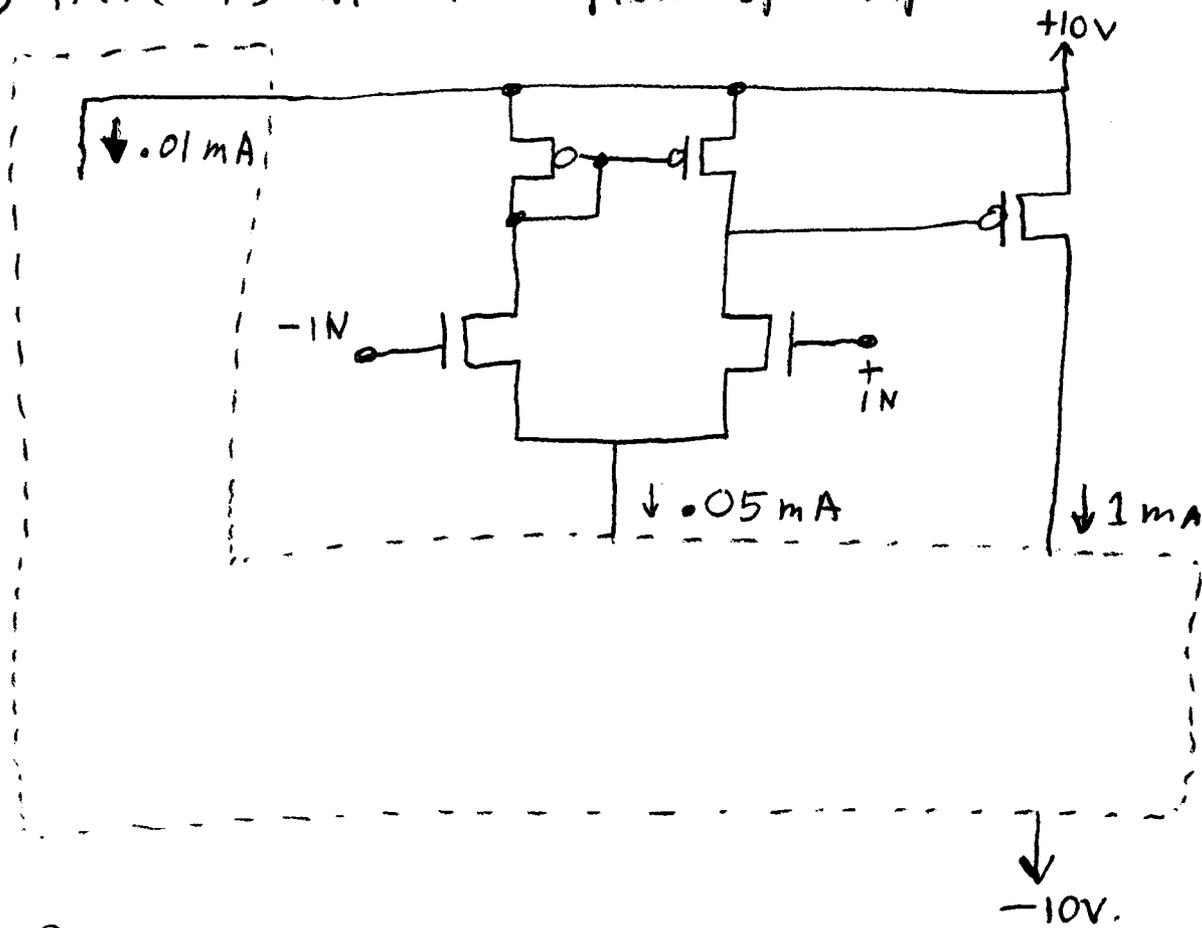

Design the circuit in the box,
using 4 N-channel MOSFETs.
No other components.

You need to complete the schematic
and determine the sizes

$$W_{\text{MIN}} = L_{\text{MIN}} = 1 \mu\text{m}$$


$$K' = 20 \frac{\mu\text{A}}{\text{V}^2}$$

$$V_{\text{TH}} = 2$$

$$\lambda = 0$$

$$I_D = \frac{1}{2} K' \frac{W}{L} (V_{\text{GS}} - V_{\text{TH}})^2$$

3

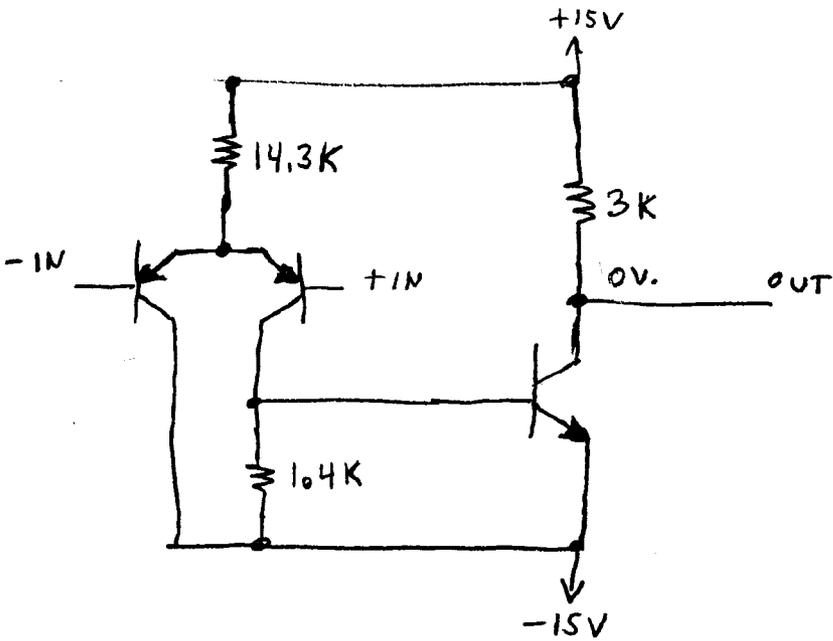

All transistors:

$$\beta = 500$$

$$V_A = \infty$$

$$g_m = \frac{I_C}{.026}$$

$$r_{\pi} = \frac{.026}{I_B}$$

What is the differential gain?
(open loop)




What is the common mode gain?



Assume it is biased correctly. Show all work.

4 Here's a one stage amplifier...

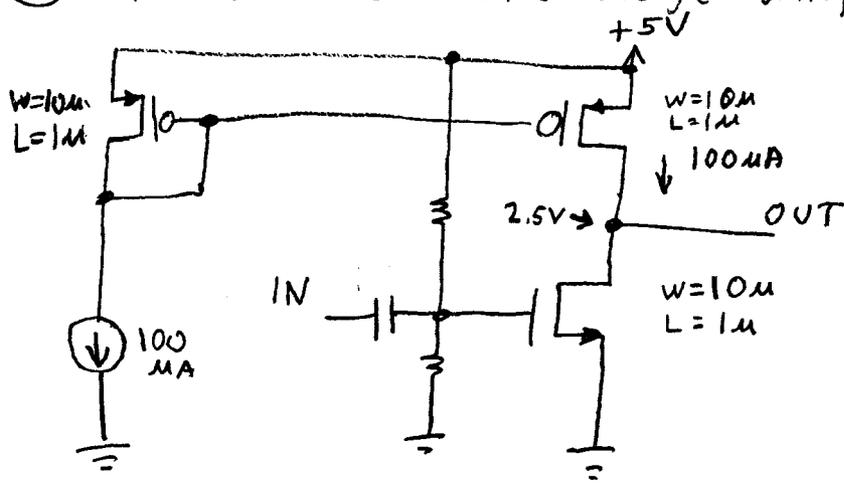


N channel device:
 $K' = 20 \frac{\mu A}{V^2}$
 $\lambda = 0.01$

P channel device:
 $K' = 10 \frac{\mu A}{V^2}$
 $\lambda = 0.01$

Both: $g_m = \sqrt{2K' \frac{W}{L} I_D}$

Assume that it is biased correctly.

What is gain $\frac{V_{out}}{V_{in}}$?

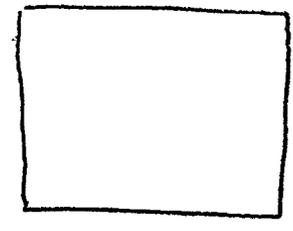

Hint: You need to find the effective R_{load} based on λ for both devices. Then find g_m . Then g_m and R_{load} will tell you the gain.