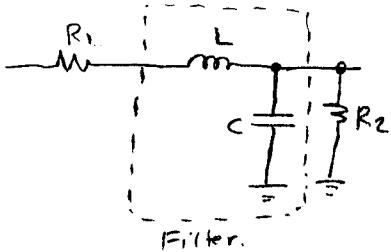


A closer look at a second order filter

Why? — Any higher order filter can be made of 1st and 2nd order sections because poles are in conjugate pairs.



Analysis:

Voltage divider approach:

$$\frac{Z_{\text{shunt}}}{Z_{\text{series}} + Z_{\text{shunt}}} = \frac{\frac{1}{R_2 + sC}}{R_1 + sL + \frac{1}{R_2 + sC}} = \frac{1}{R_1(\frac{1}{R_2} + sC) + sL(\frac{1}{R_2} + sC) + 1}$$

$$= \frac{1}{\frac{R_1}{R_2} + sCR_1 + s\frac{L}{R_2} + s^2LC + 1} = \frac{1}{s^2(LC) + s(cR_1 + \frac{L}{R_2}) + \frac{R_1}{R_2} + 1}$$

$$= \frac{R_2}{s^2(LCR_2) + s(cR_1R_2 + L) + R_1 + R_2} = \frac{\frac{R_2}{R_1 + R_2}}{s^2\left(\frac{LCR_2}{R_1 + R_2}\right) + s\left(\frac{cR_1R_2 + L}{R_1 + R_2}\right) + 1}$$

$\uparrow \quad \uparrow$
 $\frac{1}{w_0^2} \quad \frac{1}{wQ} = \frac{D}{w}$

Check: Lowpass? Yes.

$$\text{Correct gain? } = \frac{R_2}{R_1 + R_2} \quad \text{Yes.}$$

Powers of s match # of reactive elements? Yes.

(1)

Example: $f = 1 \text{ kHz}$ $D = 1.414$ ← You are given this specification.
 $R_1 = R_2 = 50 \Omega$.

"maximally flat"
"Butterworth"

more to come.

(2)

$$\omega = 2\pi f = 6283$$

Two equations:

$$\frac{1}{w_0^2} = \frac{LCR_2}{R_1 + R_2}$$

$$\frac{D}{w} = \frac{CR_1R_2 + L}{R_1 + R_2}$$

$$\frac{1}{(6283)^2} = LC(0.5)$$

$$\frac{1.414}{6283} = C(50)(0.5) + \frac{L}{100}$$

$$LC = \frac{2}{6283^2} = \frac{2}{39.4 \times 10^6} = 50.66 \times 10^{-9}$$

$$\frac{1.414}{6283} = 2SC + \frac{L}{100}$$

$$\frac{1.414}{6283} - 2500C = L$$

$$0.0225 - 2500C = L$$

$$(0.0225 - 2500C)C = 50.66 \times 10^{-9}$$


$$0.0225C - 2500C^2 = 50.66 \times 10^{-9}$$

$$2500C^2 - 0.0225C + 50.66 \times 10^{-9} = 0$$

$$C = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a} = \frac{0.0225 \pm \sqrt{506.3 \times 10^{-9} - (4)(2500)(50.66 \times 10^{-9})}}{2(2500)}$$

$$= \frac{0.0225}{5000} = 4.5 \times 10^{-6}$$
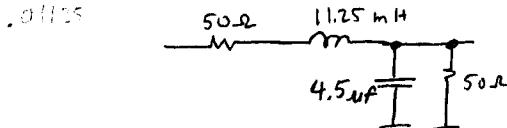
$$L = 0.0225 - 2500C = 0.01125 = 11.25 \times 10^{-3}$$



(checked with simulator $-9 \text{ dB}, -90^\circ @ 1 \text{ kHz}$) 40 dB/dec

Alternative design technique —

Design for $R = 1 \Omega$ $\omega = 1$

Then scale it.

Why? ① It's easier.

② Often tables are available.

$$\frac{1}{w_0^2} = \frac{LCR_2}{R_1+R_2}$$

$$1 = 0.5LC$$

$$LC = 2$$

$$\frac{D}{w} = \frac{CR_1R_2+L}{R_1+R_2}$$

$$1.414 = \frac{C+L}{2}$$

$$2.828 = C+L$$

$$2.828 - C = L$$


$$(2.828 - C)C = 2$$

$$2.828C - C^2 = 2$$

$$C^2 - 2.828C + 2 = 0$$

$$C = \frac{2.828 \pm \sqrt{8-8}}{2} = \frac{2.828}{2} = 1.414$$

$$L = 2.828 - C = 1.414$$

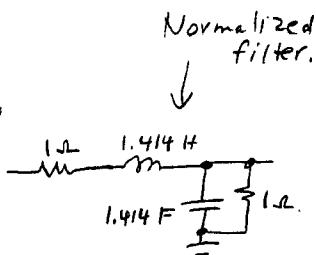


Scale Frequency — divide L and C by w

$$\frac{1.414}{6283} = 225 \mu F$$

$$225 \mu H$$

Scale Resistance
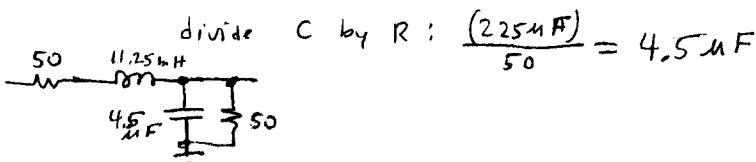
$$\text{multiply } L \text{ by } R : (225 \mu H)(50) = 11.25 \mu H$$




Poles & zeros of the normalized filter:

$$\frac{\frac{R_2}{R_1+R_2}}{s^2 \left(\frac{LCR_2}{R_1+R_2} \right) + s \left(\frac{CR_1R_2+L}{R_1+R_2} \right) + 1}$$

$$= \frac{\frac{1}{1+1}}{s^2 \left(\frac{(1.414)(1.414)(1)}{1+1} \right) + s \left(\frac{(1.414)(1)(1)}{1+1} + 1.414 \right) + 1}$$

$$= \frac{0.5}{s^2 + 1.414s + 1}$$

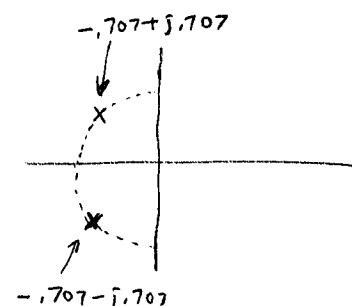

(4)

Active filters


Want to eliminate inductors.

- Two strategies:
- ① Mimic the inductor - "Gyrorator" approach.
 - ② Solve the differential equation.

Strategy ① Mimic the inductor.

"Sallen + Key" design

↑
the inventors.

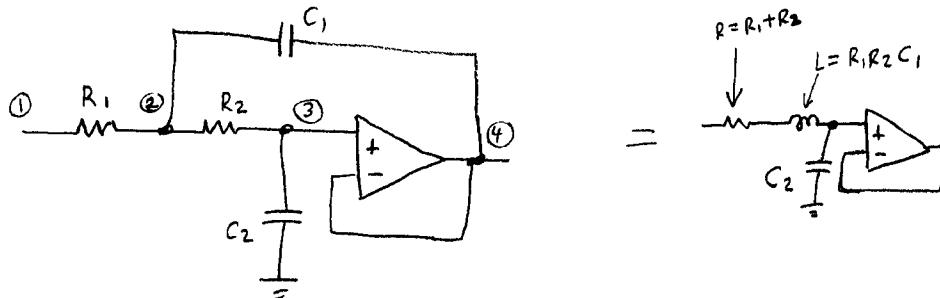

Analysis:

Node equations

$$② \frac{1}{R_1}(V_2 - V_1) + \frac{1}{R_2}(V_2 - V_3) + sC_1(V_2 - V_4) = 0$$

$$③ \frac{1}{R_2}(V_3 - V_2) + sC_2(V_3) = 0$$

$$④ V_3 = V_4$$

(5)

Group V terms ..

(6)

$$② V_1\left(-\frac{1}{R_1}\right) + V_2\left(\frac{1}{R_1} + \frac{1}{R_2} + sC_1\right) + V_3\left(-\frac{1}{R_2}\right) + V_4(-sC_1) = 0$$

$$③ V_2\left(-\frac{1}{R_2}\right) + V_3\left(\frac{1}{R_2} + sC_2\right) = 0$$

Solve ③ for V_2

$$V_2 = V_3\left(\frac{1}{R_2} + sC_2\right)(R_2)$$

$$= V_3(1 + sC_2 R_2)$$

$$\text{Subst } V_3 = V_4 \quad V_2 = V_4(1 + sC_2 R_2)$$

Sub in ②

$$V_1\left(-\frac{1}{R_1}\right) + V_4(1 + sC_2 R_2)\left(\frac{1}{R_1} + \frac{1}{R_2} + sC_1\right) + V_4\left(-\frac{1}{R_2}\right) + V_4(-sC_1) = 0$$

clean up.

$$V_1\left(-\frac{1}{R_1}\right) + V_4\left[\frac{1}{R_1} + \cancel{\frac{1}{R_2}} + \cancel{sC_1} + \frac{sC_2 R_2}{R_1} + \frac{sC_2 R_2}{R_2} + (sC_2 R_2)(sC_1) - \cancel{\frac{1}{R_2}} - \cancel{sC_1}\right] = 0$$

$$V_1\left(-\frac{1}{R_1}\right) + V_4\left[s^2(C_1 C_2 R_2) + s\left(\frac{C_2 R_2}{R_1} + C_2\right) + \frac{1}{R_1}\right] = 0$$

mult by R_1

$$V_1(-1) + V_4\left[s^2(C_1 C_2 R_1 R_2) + s(C_2 R_2 + C_2 R_1) + 1\right] = 0$$

$$\frac{V_4}{V_1} = \frac{1}{s^2(C_1 C_2 R_1 R_2) + s(C_2 R_2 + C_2 R_1) + 1}$$

Check: Low pass? Yes.

Correct gain? Yes.

Powers of s match? Yes.

Design a filter—

$$\text{"Normalized"} \quad R=1, \omega=1. \quad D=1.414.$$

$$\frac{1}{\omega_0^2} = C_1 C_2 R_1 R_2$$

$$\frac{D}{\omega} = C_2 (R_1 + R_2)$$

$$\frac{1}{s^2 + 1.414s + 1}$$


$$C_1 C_2 = 1$$

$$2 C_2 = D = 1.414$$

$$C_2 = \frac{1.414}{2} \\ = 0.707$$

$$C_1 = \frac{1}{C_2}$$

$$= \frac{1}{0.707} = 1.414$$

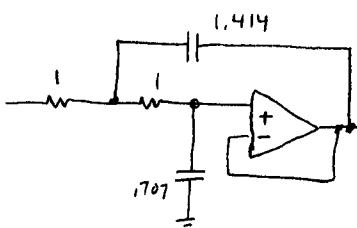

Design for 1 kHz, $D = 1.414$, $R_1 = R_2 = 10K$.

Scale f: divide C by $\omega = 2\pi f$


$$C_1 = \frac{1.414}{6283} = 225 \mu F$$

$$C_2 = \frac{0.707}{6283} = 112.5 \mu F$$

Scale R: divide C by R

$$C_1 = \frac{225 \times 10^{-6}}{10^5} = 22.5 nF$$
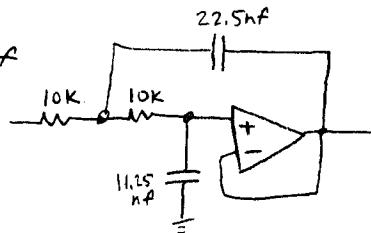
$$C_2 = \frac{112.5 \times 10^{-6}}{10^5} = 11.25 nF$$




(7)

These capacitors have ugly values.

Use 22 nF and 11 nF (standard 5% values)

Change R: We lowered both C's by .978
so increase R to 10.23 K

10.2 K is a standard 1% value.

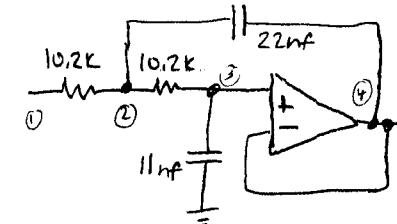

10K has actual corner at 1.03 kHz.


dB error at 1K = .2 dB

close enough.

Filters often use precision components.
(1% tolerance)

(8)

More general Low pass active filter

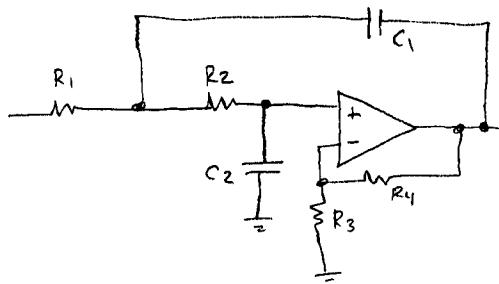

$$\frac{V_{out}}{V_{in}} = \frac{K}{s^2(R_1R_2C_1C_2) + s(R_1C_2 + R_2C_1 + R_1C_1(1-K)) + 1}$$

Good values:

(1) "Normalized" filter $\omega = 1, K = 1$
 $R_1 = 1 \quad R_2 = 1 \quad C_1 = \frac{d}{\omega} \quad C_2 = \frac{d}{2}$

$$\frac{K}{s^2(\frac{1}{\omega^2}) + s(\frac{d}{\omega}) + 1}$$

$$\frac{K\omega}{s^2 + s(d\omega) + \omega^2}$$

(2) Equal component value $\omega = 1$

$$R_1 = 1 \quad R_2 = 1 \quad C_1 = 1 \quad C_2 = 1$$

$$R_3 = 1 \quad R_4 = 2-d \quad K = 3-d$$

Then: scale frequency : $C = \frac{C_N}{\omega}$


scale resistance: $C = \frac{C_{real}}{R} \quad \text{Keep } R_1, R_2 \text{ equal.}$
 $(RC = \text{constant})$

(9)

R_3, R_4 set gain
also damping.

$$K = 1 + \frac{R_4}{R_3}$$

High pass

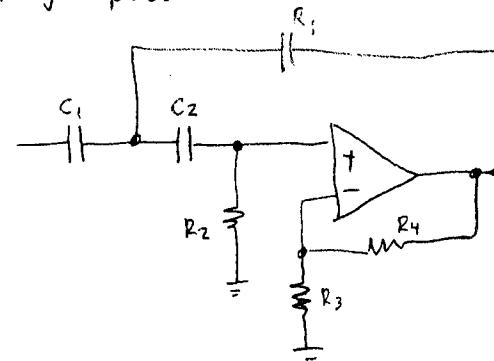

(10)

$$\frac{V_{out}}{V_{in}} = \frac{K s^2 (R_1 R_2 C_1 C_2)}{s^2 (R_1 R_2 C_1 C_2) + s (R_1 C_2 + R_2 C_1 + R_2 C_2 (1-K)) + 1}$$

Good values:

(1) Normalized, unity gain:

$$\omega = 1 \quad K = 1$$

$$C_1 = 1 \quad C_2 = 1 \quad R_1 = \frac{d}{2} \quad R_2 = \frac{2}{d}$$

$$\frac{K s^2 / \omega^2}{s^2 / \omega^2 + s(d/\omega) + 1}$$

$$\frac{K s^2}{s^2 + s(d\omega) + \omega^2}$$


(2) Equal component value

$$C_1 = 1 \quad C_2 = 1 \quad R_1 = 1 \quad R_2 = 1$$

$$R_3 = 1 \quad R_4 = 2-d \quad K = 3-d$$

Band pass - multiple feed back (Low Q)

(11)

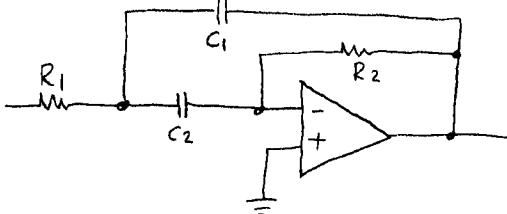

$$\frac{V_{out}}{V_{in}} = \frac{-s(R_2C_2)}{s^2(R_1R_2C_1C_2) + s(R_1C_2 + R_2C_1) + 1}$$

$$= \frac{\frac{Ks}{s^2 + s(d\omega) + \omega^2}}{d + \frac{1}{\omega}}$$

Good values: ($\omega = 1$)

$$C_1 = 1 \quad C_2 = 1 \quad R_1 = \frac{1}{2Q} \quad R_2 = 2Q \quad (R_1R_2 = 1)$$

$$\frac{Ks}{s^2 + s(d\omega) + \omega^2} = d + \frac{1}{\omega}$$

Gain at $s^2 = -1$ ($s = j$):

$$\frac{-j(R_2)}{-1(R_1R_2) + j(R_1 + R_2) + 1} = \frac{-R_2}{2R_1}$$

$$\frac{-j(2Q)}{-1 + j(\frac{2}{2Q}) + 1} = \frac{-2Q}{\frac{2}{2Q}} = \frac{-4Q^2}{2} = -2Q^2$$

Gain and Q
are related.

Example: $f = 1 \text{ kHz}$ bandwidth = 100 Hz
 $Q = 10$

(12)

Normalized:

$$C_1 = 1 \quad C_2 = 1 \quad R_1 = \frac{1}{20} \quad R_2 = 20 \quad R_1R_2 = 1$$

Scale Frequency

$$C_1 = C_2 = \frac{1}{6283}$$

Scale to $R_1 = 1 \text{ k}$, then $R_2 = 400 \text{ k}$ $R_1R_2 = 400 \times 10^6$
 $\sqrt{R_1R_2} = 20 \text{ k}$

$$C_1 = C_2 = \frac{1}{(6283)(20 \text{ k})} = 7.958 \text{ nF}$$

Actually use $C_1 = C_2 = 10 \text{ nF}$

$$R_1 = 7.958 \text{ k} \quad \left\{ \begin{array}{l} 7.89 \text{ k} \\ 8.05 \text{ k} \end{array} \right. \leftarrow 1\% \text{ std values}$$


$$R_2 = 318.3 \text{ k} \quad \left\{ \begin{array}{l} 316 \text{ k} \\ 323 \text{ k} \end{array} \right. \leftarrow 1\% \text{ std values}$$

$$\sqrt{R_1R_2} = 50.33 \text{ k}$$

$$\sqrt{R_1R_2} = 50.44 \text{ k}$$

4 op-amp filter (high Q)

(13)

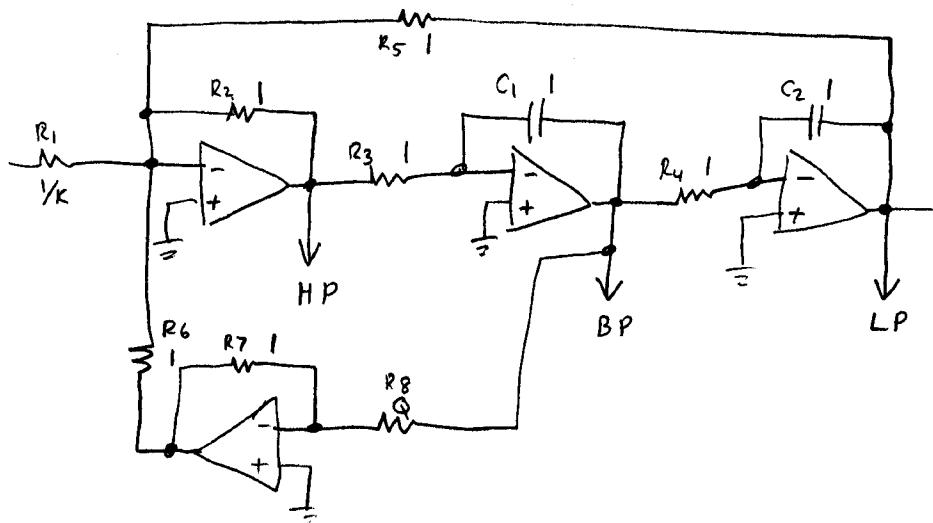

$$Q = \frac{R_8}{R_7} \quad \omega_0 = \frac{1}{R_3 R_4 C_1 C_2}$$

Good values:

$$R_3 = R_4 \quad C_1 = C_2$$

$$R_2 = R_5 = R_6$$

$$R_1 = \frac{R_2}{K}$$