

Amplitude Modulation (and variants)

3D-1

To send information, modulate the amplitude of a carrier.

As opposed to ...

"Angle" modulation -

To send information, modulate the angle (phase, frequency, etc.) of a carrier. → Chapter 5

Chapter 4 ---

4.1 Introduction.

Variants of AM

4A 4.3 - Real AM, the simplest.

Theory -

Transmitters

Envelope detectors

4B 4.2 - Double sideband - suppressed carrier

Theory

Transmitters

Synchronous detectors

4.4 - Quadrature AM - phase tricks.

⇒ 4C - AM Lab?

4D 4.5 Single Sideband

Theory

Hilbert transform

Filter method

Phase shift method

How to make a circuit with $G(\omega) = j$
 $(G(\omega) = j\omega \text{ is too easy!})$

5A 4.6 Vestigial sideband - TV bandwidth hack

Theory

generation

detection

AM Circuits, design tricks, etc.

5B 4.7 Carrier Acquisition

Synchronous detection

pilot signal

Phase locked loops { voltage controlled oscillator
phase detection
"capture"

5D

Suppressed carrier tricks.

Signal Siphoned method

phase locked loop.

single sideband, oops.

6A 4.8 Superheterodyne receiver

Mixers

Filters

Images.

6B 4.9 Television

Raster scan video

Sync

Color


Sound track

6C - AM Test

Recall --

Frequency shifting.

To transmit:

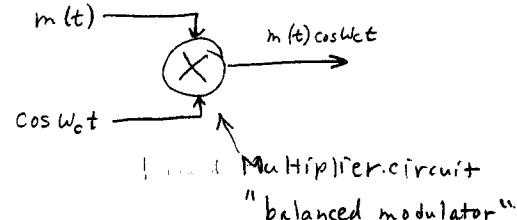


Has 2 inputs —

output is the product of the inputs.


$$m(t) \cos w_c t \Leftrightarrow \frac{1}{2} [M(w+w_c) + M(w-w_c)]$$

Frequency domain

input spectrum:

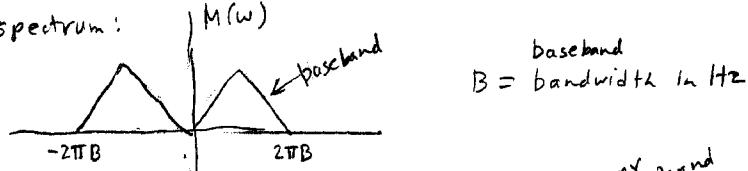


transmitted spectrum:

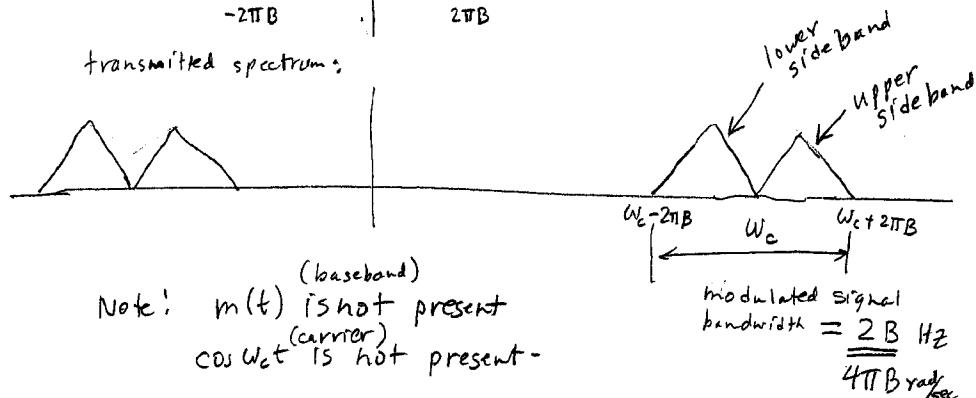


3D-3

Time domain:

$$m(t) =$$

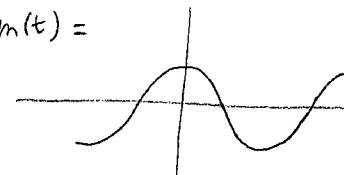

$$m(t) \cos w_c t$$

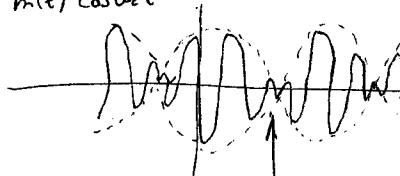


w_c contained in envelope defined by $m(t)$

phase reversal

3D-4

To receive:

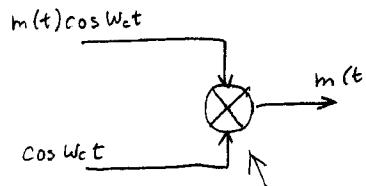Need to frequency shift again, back down to the baseband.



multiplier circuit
"product detector"

Problem: how to generate $\cos w_c t$.

Note: $\sin w_c t$ won't work !!!
Output will be $\underline{\underline{0}}$.

Brute - Force approach.—


3B-5

How to generate $\cos \omega_c t$?




Transmit it!

Idea: Level shift $m(t)$ (add a DC component)

so it is always positive.

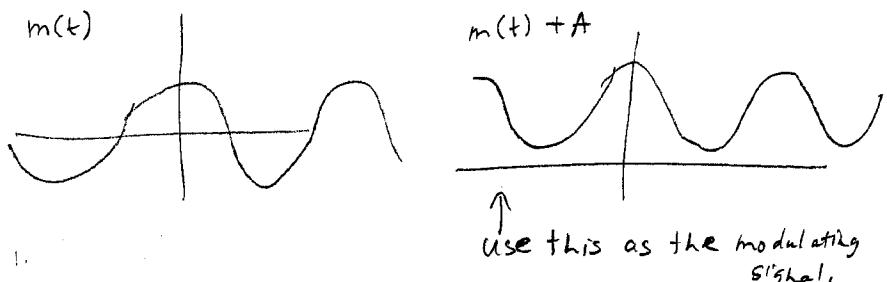

$(m(t) + A)(\cos \omega_c t)$:

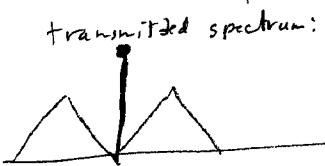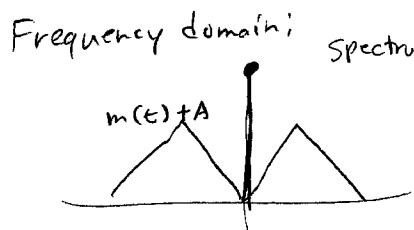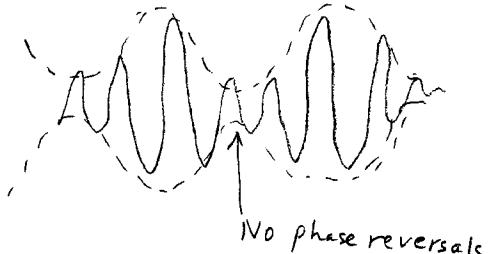


ω_c is present.

AM demodulation

3D-6

It is simple now!

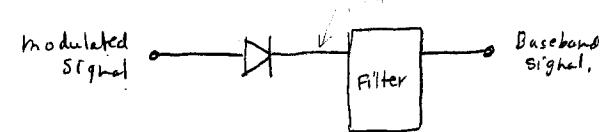

Rectifier detector:

IN



After diode



After Filter



takes average value,
filtering out carrier,

Then use a coupling capacitor to center it, so $V_{dc} = 0$



The filter is simple —


usually a simple RC will do —

because carrier frequency is much higher
than baseband bandwidth!

Envelope detector.


3D-7

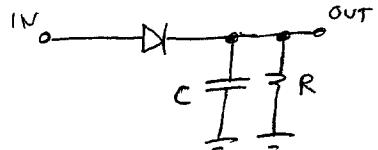Same except to use a capacitor input filter—
the cap charges to the peak value;




RC is chosen for proper filtering.

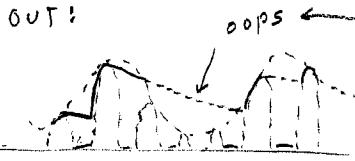If time constant too long,
it won't follow the envelope.)



A simple AM radio receiver:

3D-8

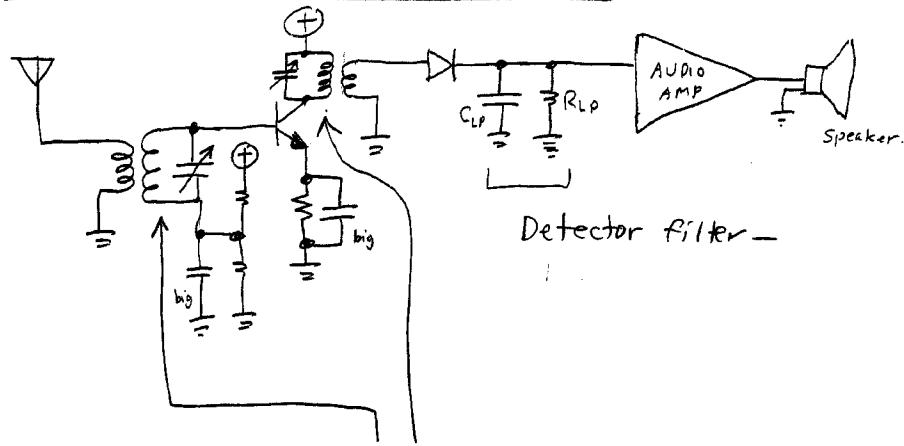

Detector filter—

2 tuned circuits—

RF filter to select frequency to receive.

Transmitting AM

3D-9

→ They don't use balanced modulators!


Idea: Since the carrier is a single frequency, it is ok to use a "bad" amplifier then filter it.

Class C amplifier:


Drive it to clipping.

Bias it so it is off with no drive.
Filter the output.

Example:

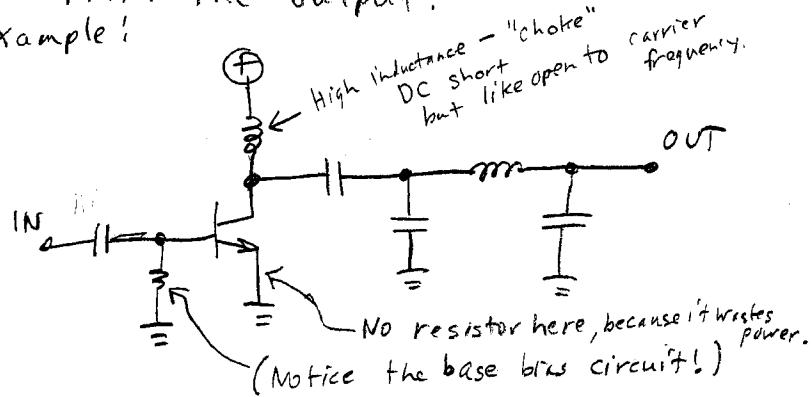

IN:

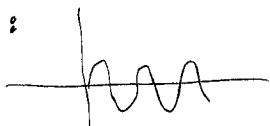


OUT (without filtering)




Using historically correct devices:

Vacuum tube:

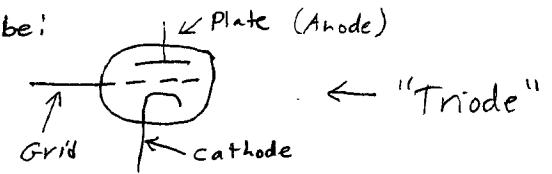

Construction:

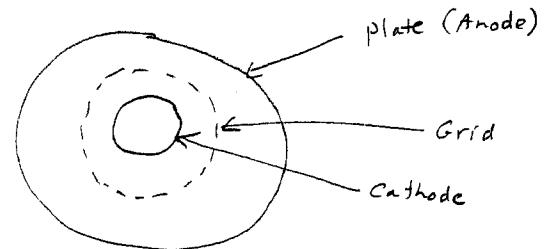

Cathode is heated, emits electrons.

Attracted to plate by positive charge
Grid controls flow of electrons.


(like gate controls a FET).
Normally, current flows. Negative bias on grid
reduces current.

class C amplifier —
is always clipping,
so output depends on supply voltage


→ Apply modulation in
series with power supply.

3D-10

"Plate modulated" AM transmitter 3D-11

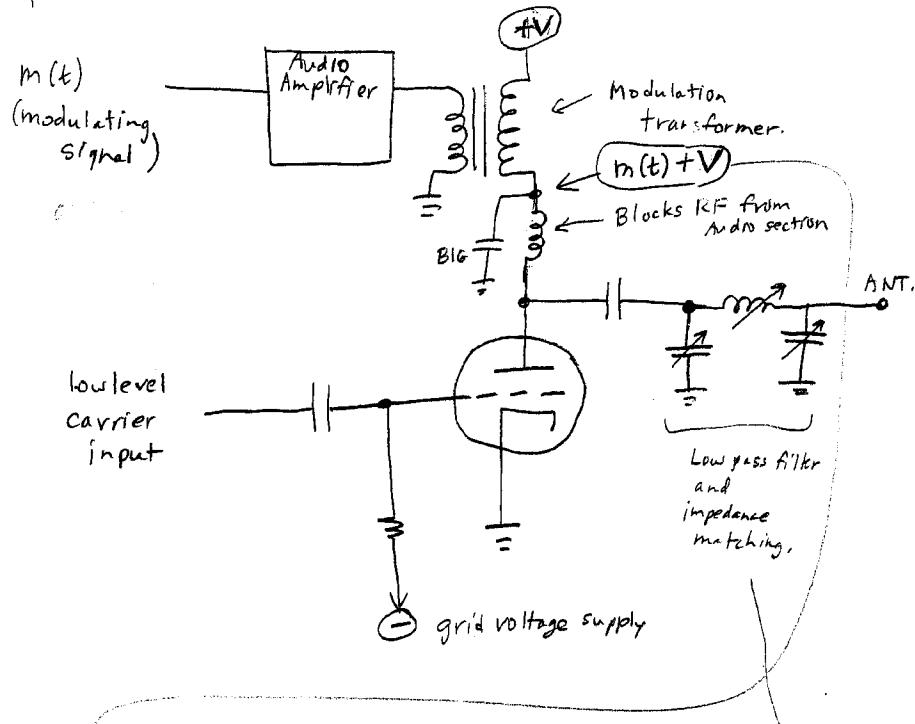

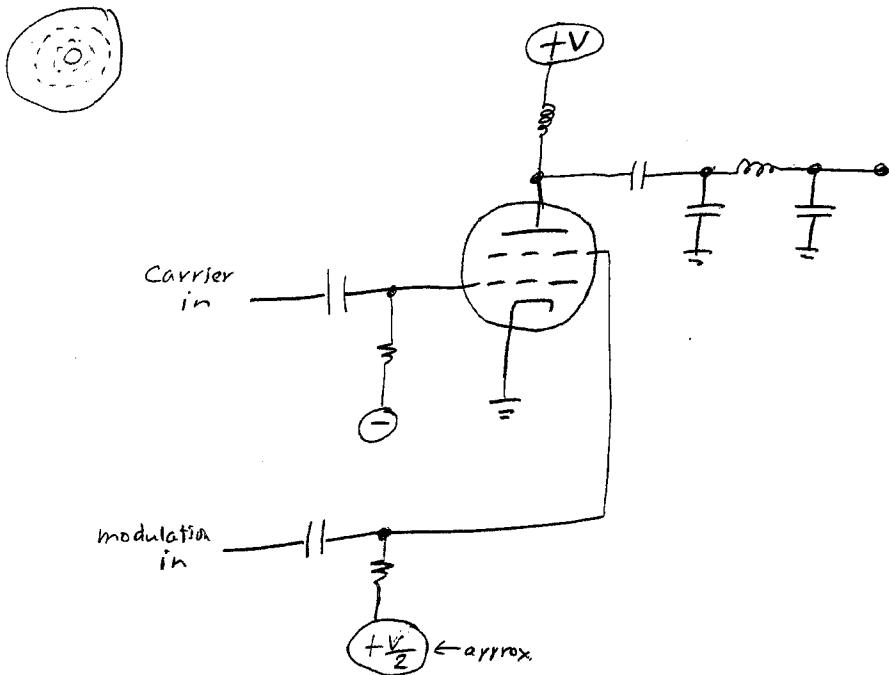"Screen modulated" AM transmitter — 3D-12
use a tube with 2 grids (tetrode)



"Screen" voltage adjusts the gain and current
— so it modulates —

$m(t)$ is a LARGE version
of the modulating signal —

$$\text{peak-to-peak voltage} = \underline{\underline{2V}} \\ (2000 \text{ Volts})$$

Peak voltage at plate is 4X supply.