

Generating FM.


7D-1

Direct method — "voltage controlled oscillator"

See 7A-2 for schematic.

- Advantages: Capable of large modulation
 May not be necessary to use multipliers.
- Disadvantages: Poor carrier frequency stability.

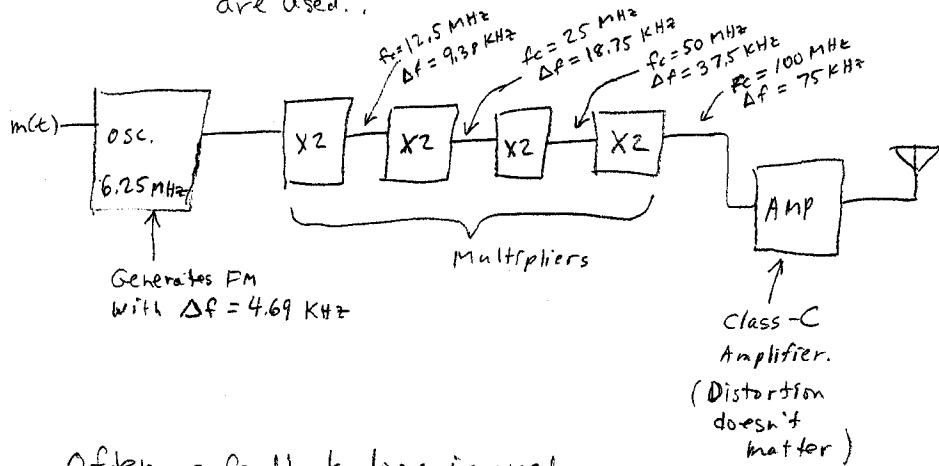To get larger frequency deviation, often multipliers are used.:




Often a feedback loop is used to stabilize the frequency.

Multiplier is either:

- (A) — class C amplifier with output tuned to harmonic.
- (B) Full wave rectifier, and tuned circuit

Armstrong's method

7D-2

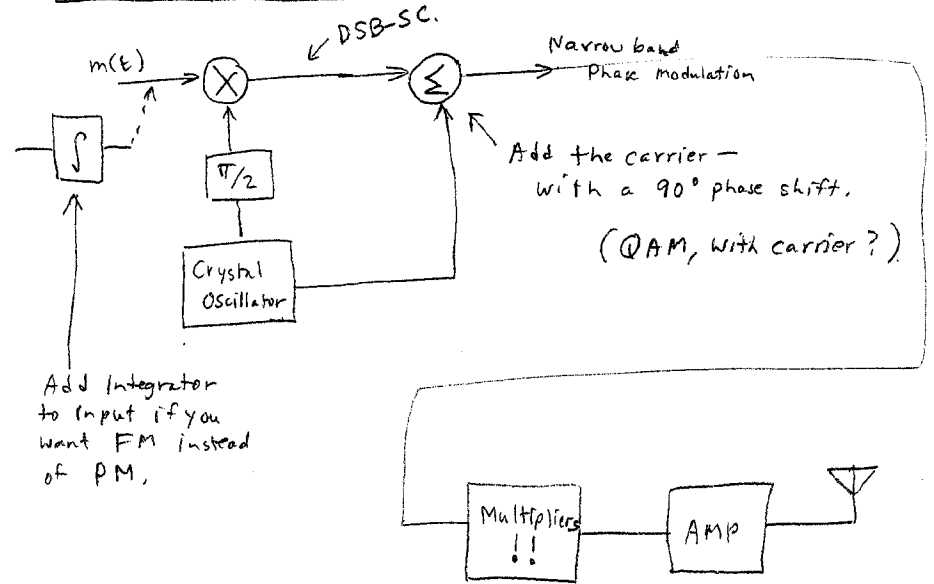

Based on the assumption that higher order side bands can be ignored. — Only the first is needed. — Very low modulation levels.

Distortion may be high ---

(3rd harmonic of m(t))	$\propto \frac{\beta^2}{4}$	$\frac{\beta}{4}$	$\frac{\beta^2}{4}$
(text p. 230)		→ .5	.06 = 6%
communications grade only		→ .1	.0025 = .25%
		→ .2	.01 = 1%
"mid-f"		→ .05	.0006 = .06%
decent quality.			

Reason for high distortion ---
 Truncation of power series.

More -- Armstrong's method --

7D-3

β is highest at lowest mod frequencies --

so (Example) -- Allow 1% distortion at 50 Hz

This means $\max \beta = .2 \frac{\Delta f}{f_m}$

$$\Delta f = \beta f_m = (.2)(50) = 10 \text{ Hz.}$$

To get 75 KHz deviation --

need to multiply by 7500

This means the starting f_c (for 10 Hz deviation)

$$\text{must be } \frac{100 \times 10^6}{7500} = \underline{\underline{13 \text{ kHz}}}$$

This is too low for

$$f_m = 15 \text{ kHz. (mono)}$$

MUCH too low for

$$f_m = 53 \text{ kHz (stereo).}$$

Solution (?)


Use a heterodyne technique.

Start with a reasonable frequency --
(200 kHz)

Do some of the multiplication.

Convert it down (heterodyne --
or frequency shift)

Do more multiplication.

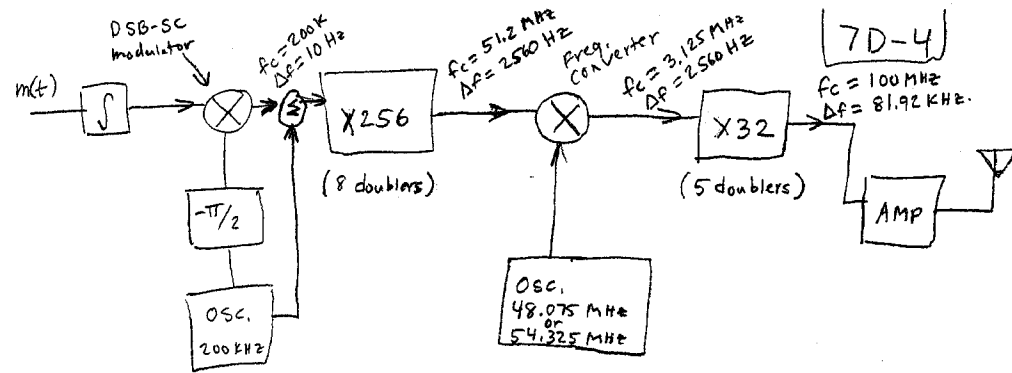

Actually use initial $\Delta f = \frac{75000}{8192} = 9.15 \text{ Hz.}$

Advantages --

Very stable frequency (f_c) -- crystal oscillators.

Disadvantages --

Need many multiplier stages.

Possibly high distortion.

Notes --

Not often used in broadcast transmitters.

More common in communications transmitters.

Consider -- $f_c = 160 \text{ MHz}$ $\Delta f = 5 \text{ kHz}$

$$300 \text{ Hz} < f_m < 3000 \text{ Hz.}$$

6% distortion is ok at 300 Hz.

$$\text{Need } \beta = \frac{5000}{300} = 16.67$$

Can do $\beta = .5$ -- so need to multiply by $\frac{16.67}{.5} = 33.33$

$$\text{Use initial } f_c = \frac{160 \text{ MHz}}{32} = 5 \text{ MHz.}$$


This is reasonable.

≈ 32
5 doublers.

Demodulation

7D-5

All FM receivers use "limiters" to remove the AM component.

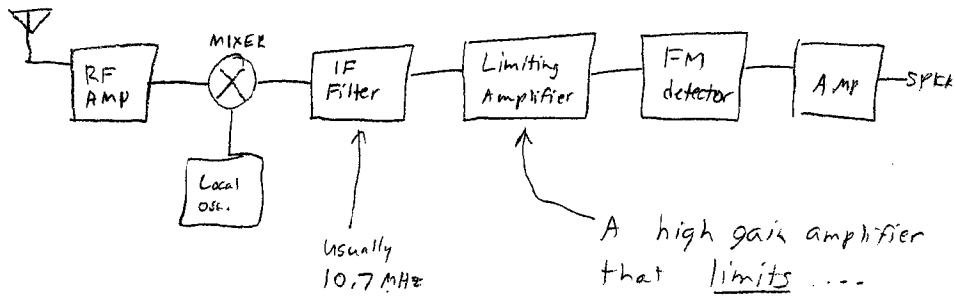


Usually 10.7 MHz

A high gain amplifier that limits ...
Driven to clipping - so the output is always the same amplitude.

Slope Detection

7D-6

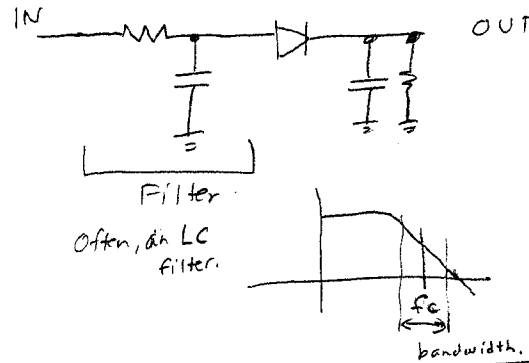
Use a filter - so the signal is on the slope. Then use an envelope detector.



Filter creates AM signal from FM.

Double-tuned discriminator -

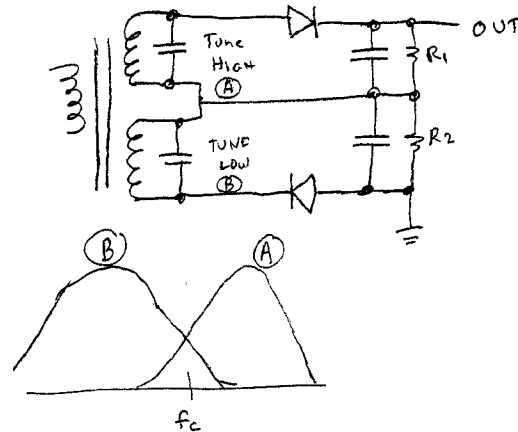Use 2 slope detectors, one tuned on each side --



Even order distortion cancels.

Outputs are combined (sum) in a differential rectifier


When $f = f_c \dots V_{R1} = -V_{R2}$

so the sum = 0

$f \neq f_c$ - the voltages are different, giving output.

Foster - Seeley discriminator

7D-7

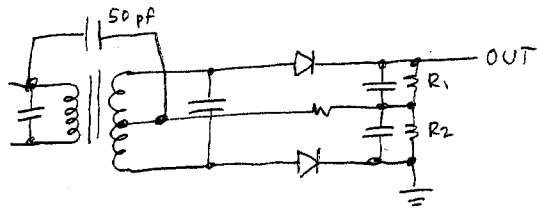


$V_{out} = \text{sum of voltages on } R_1 \text{ \& } R_2.$

When $f = f_c$, secondary voltage is 90° out of phase with primary voltage.

$V_{R1} = V_{R2}$ - so they cancel.

$f \neq f_c$ - it is not 90° , so you get output.

Ratio detector

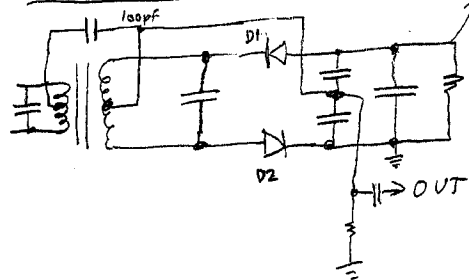

AGC voltage

Diodes polarized so voltages add -

Equal when $f = f_c$

When $f \neq f_c$,

Audio output = ratio of contributions of D_1 & D_2 .

Advantages:


Rejects AM

Can get away without limiter.

(but still needs AGC, or something to control input amplitude)

Phase-Locked loop

7D-8

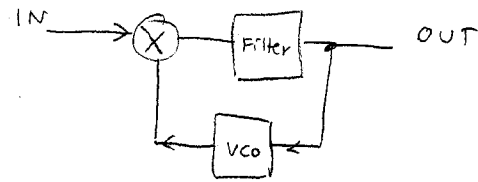

VCO tracks input, maintaining 90° error.

"OUT" is the error voltage, used to tune VCO, is also the recovered modulation.

"Filter" holds the value of OUT.